

# **CSE 260M / ESE 260**

# **Intro. To Digital Logic & Computer Design**

Bill Siever  
&  
Jim Feher



# This week

- Thursday:  
Studio — Here / Seigle 301
- Hw#5 posted was supposed to be posted by late Friday
  - *Was actually* Monday. Due Sunday at 11:59pm
  - Verilog!




# Chapter 5 & 6



# Ripple Adder

 
- Example: 1111 + 0001
- As a traditional math problem:

$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$





# Info in circuit

 

- As values in a circuit

0	0	0	0
1	1	1	1
-	0	0	1
-	-	-	-
0	0	0	0

<= Carry  $i-1$  connected to carry in of  $i$

<= "A"

<= "B"

<= "Sum"



# Info in circuit: Initial

- As values in a circuit:

```
    0 0 0 0    <= Carry i-1 connected to carry in of i
    1 1 1 1    <= "A"
+   0 0 0 1    <= "B"
-----
    0 0 0 0    <= "Sum"
```



# Info in circuit: After 1st "Sum" update

- As values in a circuit:

$$\begin{array}{rcccc} 0 & 0 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{"A"} \\ + & 0 & 0 & 0 & 1 & \leq \text{"B"} \\ \hline 1 & 1 & 1 & 0 & \leq \text{"Sum"} \end{array}$$



# Info in circuit: After 2nd "Sum" update

- As values in a circuit:

$$\begin{array}{rcccc} 0 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{"A"} \\ + & 0 & 0 & 0 & 1 & \leq \text{"B"} \\ \hline 1 & 1 & 0 & 0 & \leq \text{"Sum"} \end{array}$$



# Info in circuit: After 3rd "Sum" update

- As values in a circuit:

$$\begin{array}{rcccc} 1 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{"A"} \\ + & 0 & 0 & 0 & 1 & \leq \text{"B"} \\ \hline 1 & 0 & 0 & 0 & \leq \text{"Sum"} \end{array}$$



# Info in circuit: After 3rd "Sum" update

- As values in a circuit:

$$\begin{array}{rcccc} 1 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{"A"} \\ + & 0 & 0 & 0 & 1 & \leq \text{"B"} \\ \hline 0 & 0 & 0 & 0 & \leq \text{"Sum"} \end{array}$$



# Ripple Adder: Total Time

- $N$  bits: Worst case scenario is ripple through all  $N$ 
  - If  $T_c$  is the propagation delay through the Carry  
=  $N \cdot T_c$
  - Dictates things like maximum clock cycle for any paths/loops that use addition
  - Lots of things rely on addition!



**JLS**

**Wikipedia Animation**



# Carry Look-Ahead

- Divide large addition into  $n$ -bit blocks
- Within each block, determine if what each column would with a carry-in to the column

- Would it “Generate” a carry? ( $g_x$ )


$$\begin{array}{r} ? \quad \leq \text{Carry in} \\ a \quad \leq \text{“A”} \\ + b \quad \leq \text{“B”} \\ \hline s \quad \leq \text{“Sum”} \end{array}$$

- Would it merely “Propagate” the carry? ( $p_x$ )

- Can the carry-out be represented in terms of  $a_x$ ,  $b_x$ ,  $cin_x$ ,  $g_x$  and  $p_x$ ?




# Building a Block (of 4)

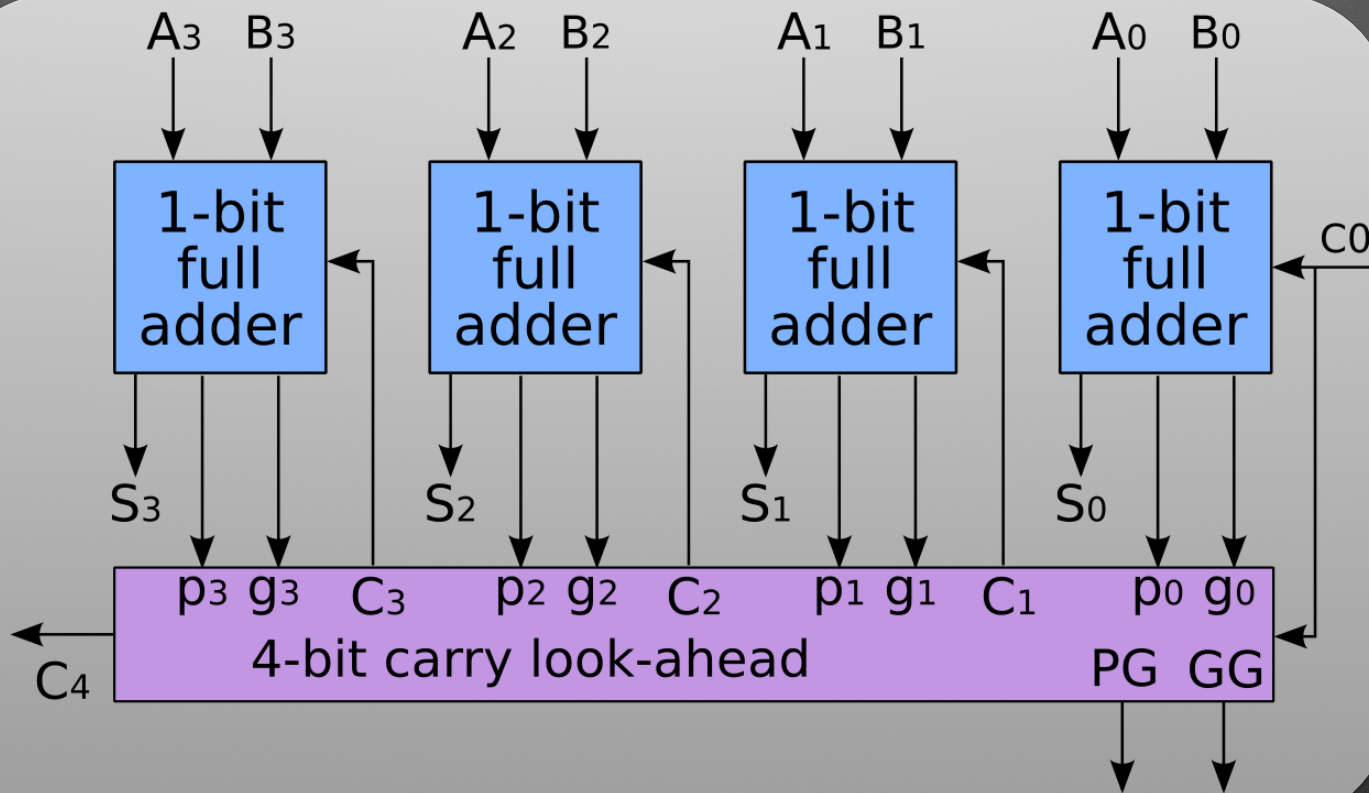



# Extend “prediction” to block

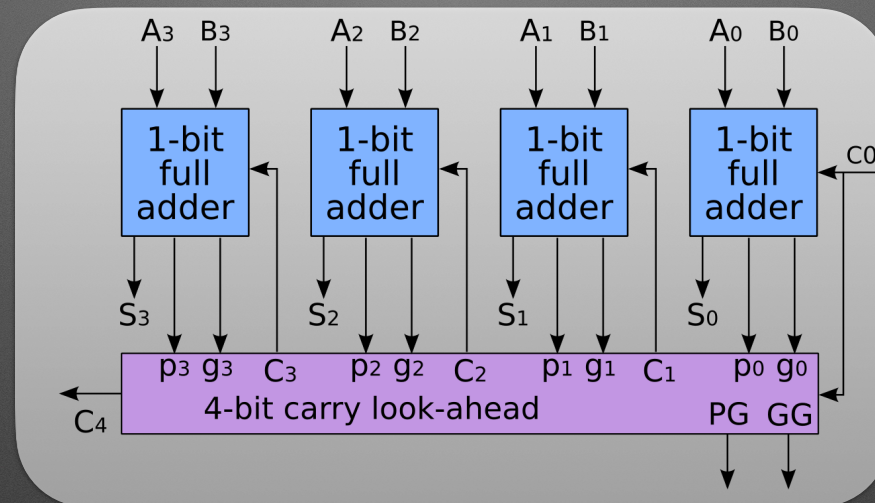


$$P_{block} = P_3 \cdot P_2 \cdot P_1 \cdot P_0$$

$$G_{block} = G_3 + P_3 \cdot (G_2 + (P_2 \cdot (P_1 \cdot G_0)))$$




# Block "Prediction"

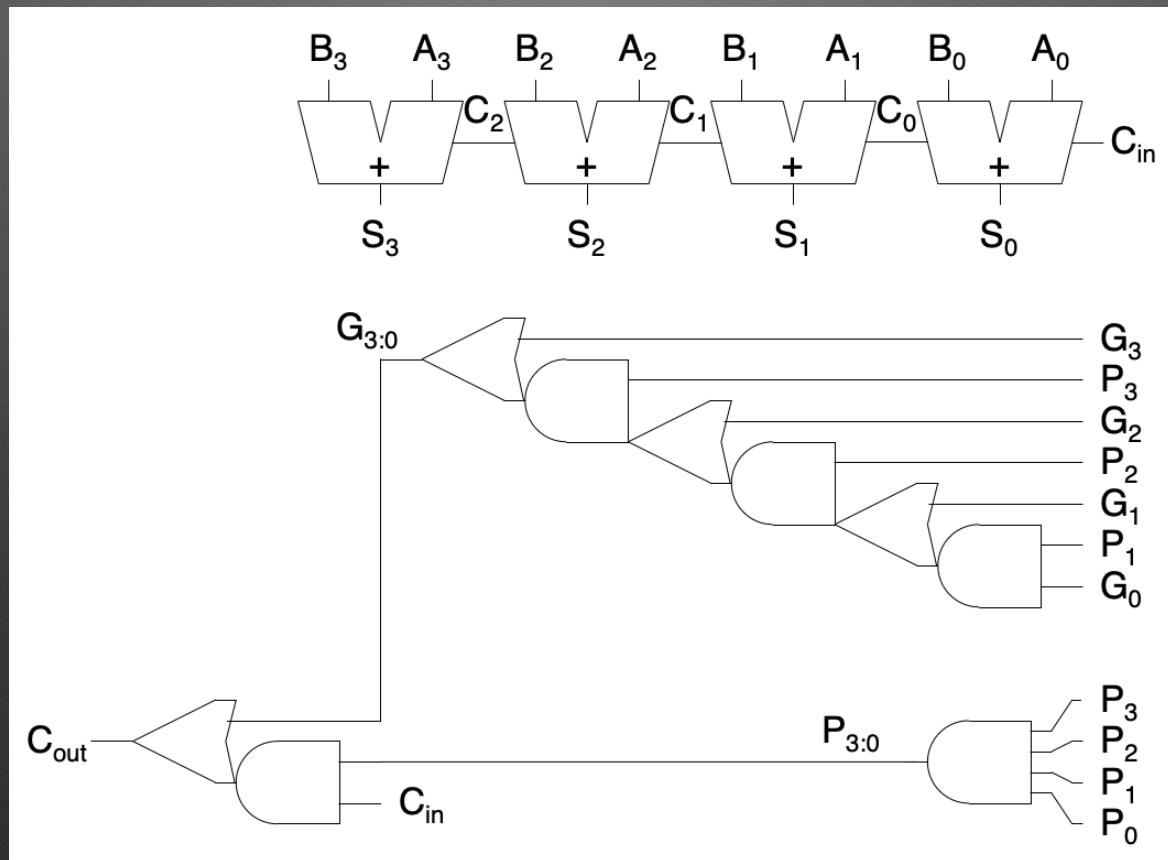



# Ripple in 4 block, 16-bit CLA

 




# Trade off: Logic vs. Time

- CLA and other tricks (Prefix adder) add logic to reduce time
- Degenerate Case: A look-up table (full sum-of-products equation)
  - How many layers of logic? (Nots, ands, ors)?
- To estimate complexity, how many rows and output columns are in a table to add two, 8-bit numbers?
  - Approximately how many AND gates?  
Approximately how many OR gates?  
Estimate the number of inputs that may be needed on OR gates


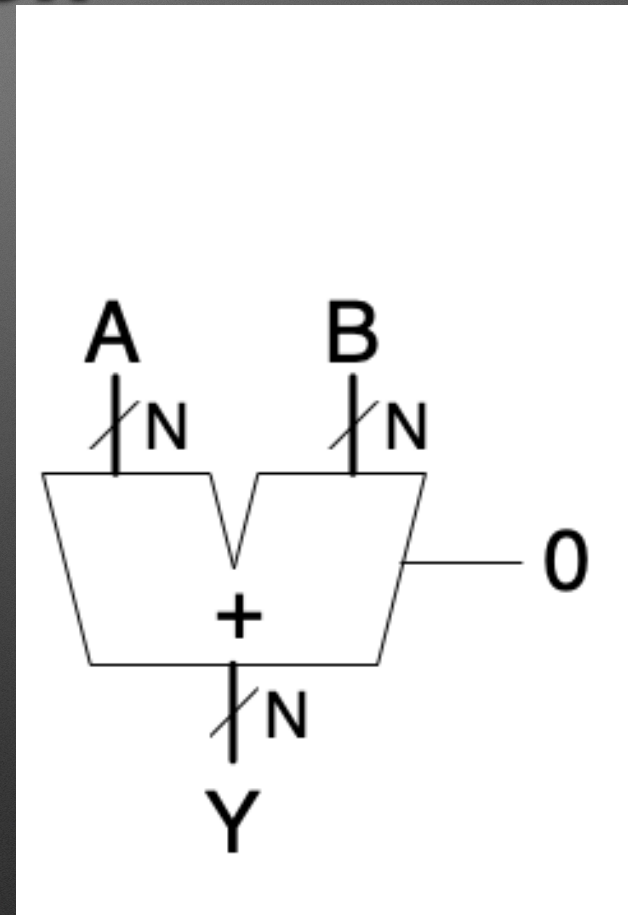
# Subtraction


- The beauty of 2's complement
- $A - B = A + \bar{B} + 1$




 
# Subtraction


- The beauty of 2's complement
- $A - B = A + \bar{B} + 1$




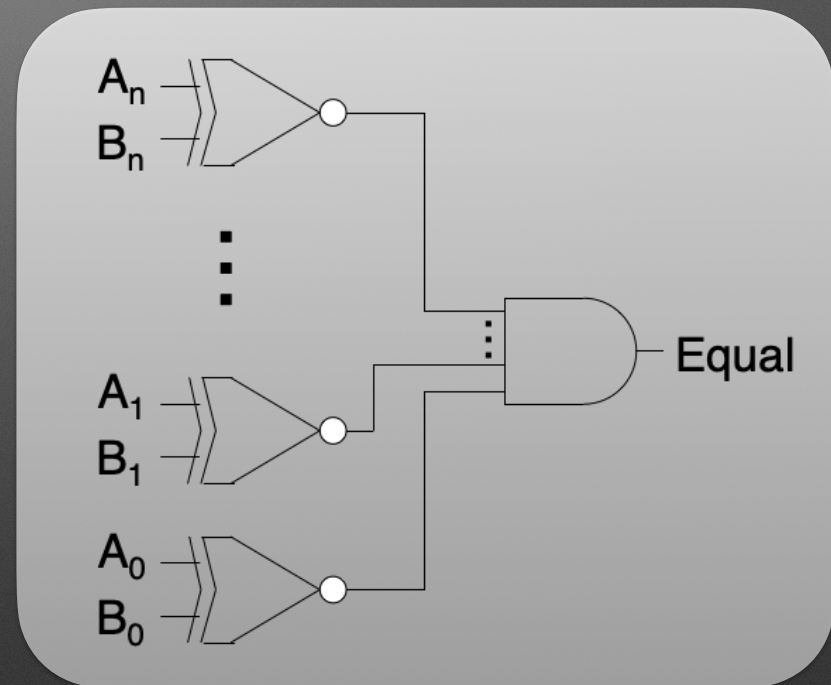
# Comparisons

- Equality
  - Easy: Are any bits different?
- Equal to zero?
- ?






# Comparisons

- Less than (signed): Is  $A < B$ ?
- Leverage Subtraction:  $A < B$  is equivalent to  $A - B < 0$ 
  - Subtract and check result
    - General: Is  $A - B$  negative?
    - But...large numbers can “overflow”.  
Need to consider overflow and signs of  $A$  &  $B$


 
# ALU: Arithmetic Logic Unit

- “Heart” of CPU: Does the computation stuff.
- Basic operations
  - Addition
  - Subtraction
  - Bitwise AND
  - Bitwise OR
  - Comparison (<)






# ALU: Arithmetic Logic Unit

- “Heart” of CPU: Does the computation stuff.

- Basic operations

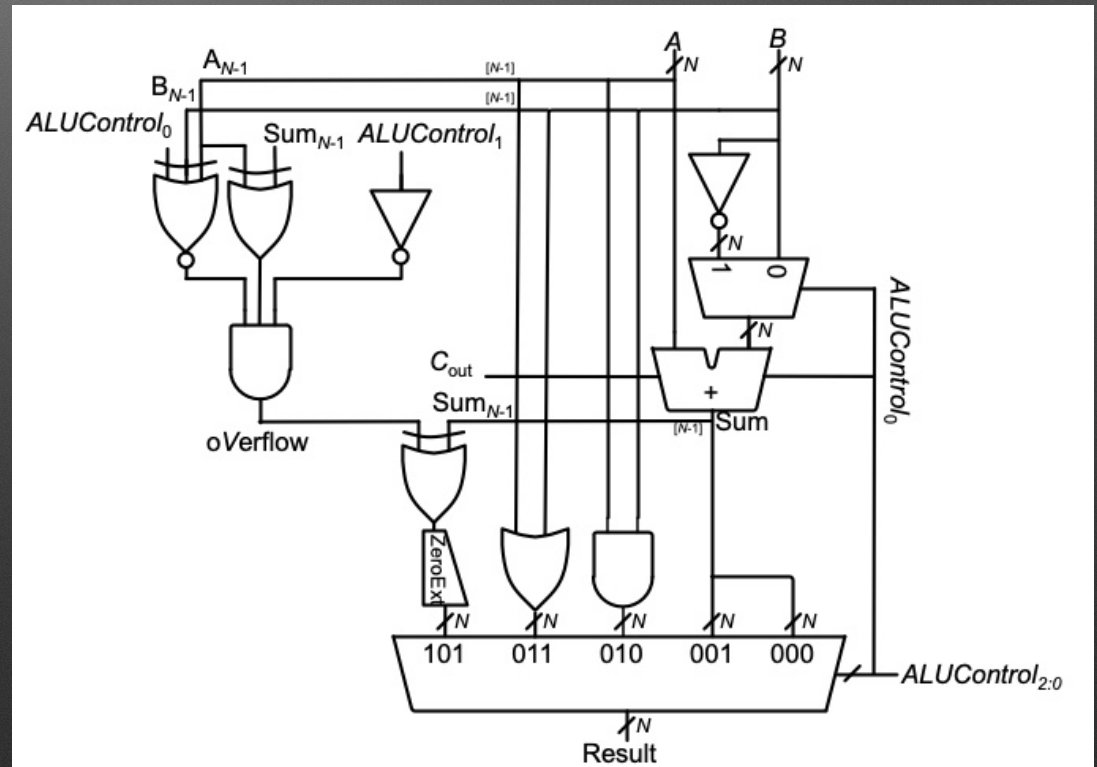- Addition: 000
- Subtraction: 001
- Bitwise AND: 010
- Bitwise OR: 011
- Comparison (<): 101





# Memory / Storage

- Common types
  - Static Random Access Memory (SRAM)
  - Dynamic Random Access Memory
  - Read Only Memory (contents can't be easily changed)



# Memory / Storage

- General Approach
  - Store in a 2D grid of elements
  - Call each row a “word”
  - Each row has an index to access the content of the entire row
  - Concept: Computer programming
    - An Array (List) is a representation of memory



# RAM: SRAM vs. DRAM



# SRAM vs. DRAM

- S = “Static”/Unchanging (well, only changing when requested!)
  - Could be build from D Flip Flops (or similar “self-reinforcing” circuits)
- D = Dynamic: Values fade if not refreshed
- RAM: “Random Access”
  - About performance of reading/updating
  - Time take (*propagation delay*) does not depend on index requested




# ROM

- Read Only
  - But still “Random Access” performance
- Fixed look-up table. Could be built with combinational logic!
  - Earlier example of “adder” could just be a ROM


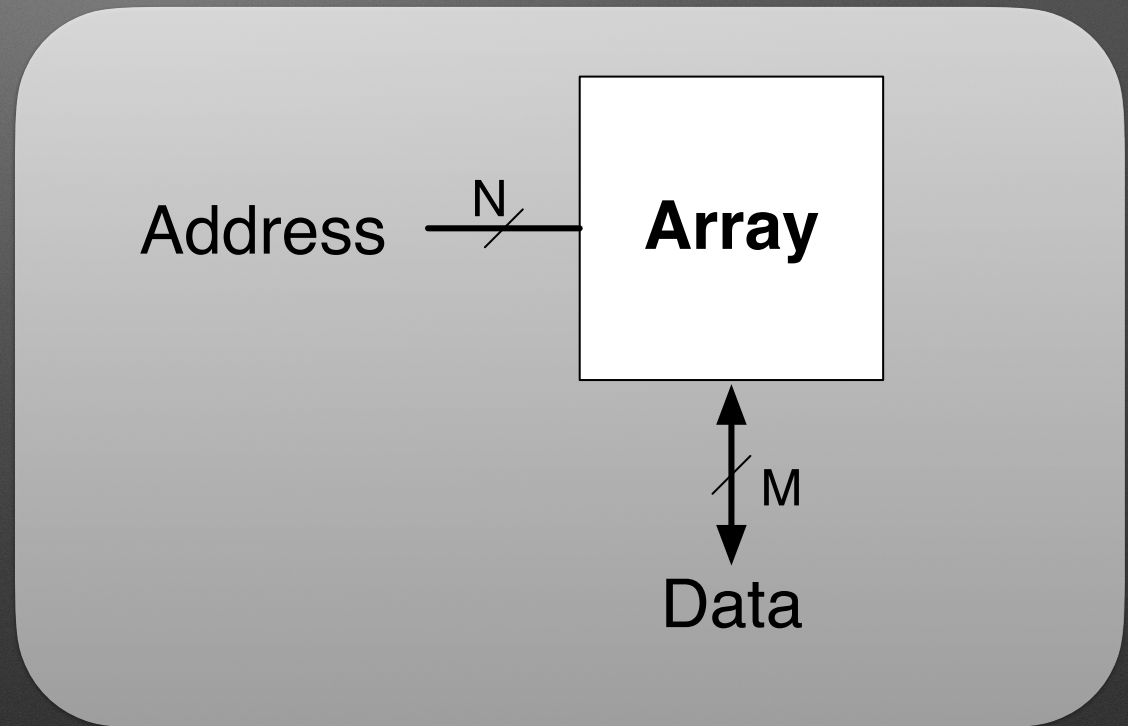
# Reading Memory


- $M$  = Word size
- $N$  = “address size”
- How many total bits are stored?




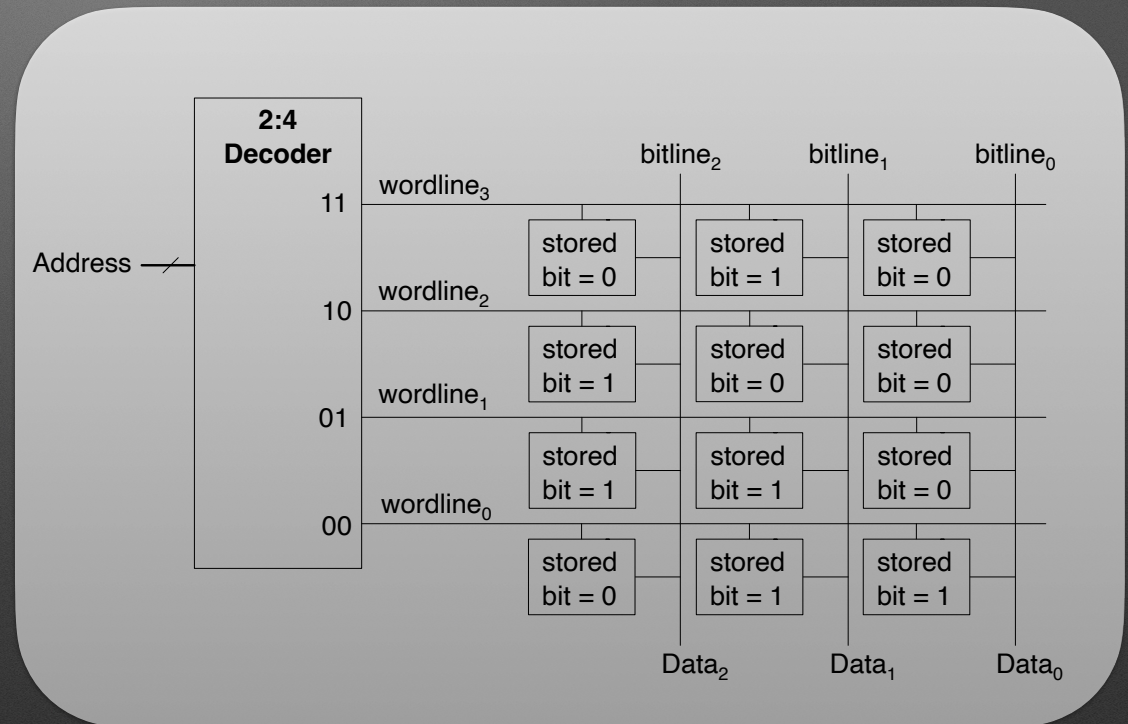
# Memory Structure


- One approach
  - Bits are “enabled” to connect to shared output line




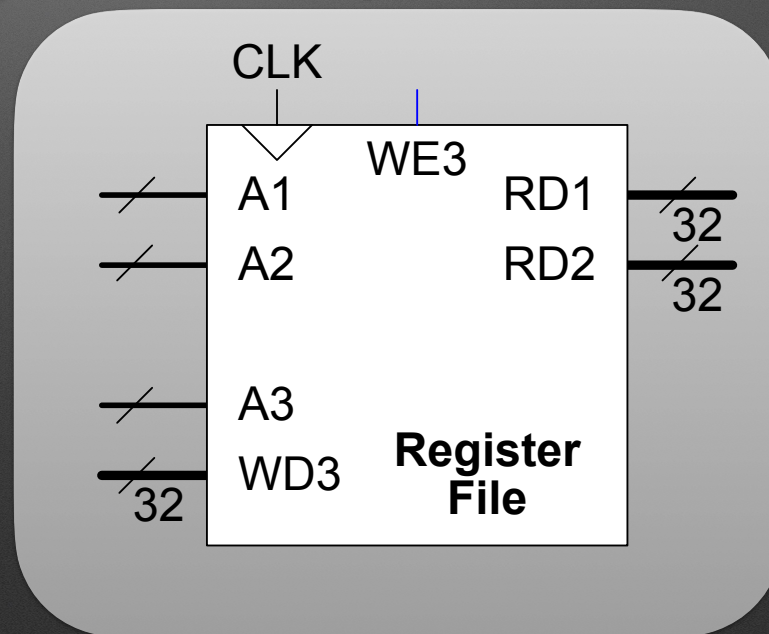
# ALU Operations

- Need TWO inputs: need a memory structure that provides two values (i.e. dual output ports)
- The “Register File”
- Also supports writing (updating)





# **JLS Register File (W/ D Flip Flops)**



# FPGA

- Field Programmable
- Gate Array
  - Lattice iCE40 UP5k: Architecture Overview
    - RAMs, (Dual and Single Port)
    - Look Up Tables (LUTs): 4 inputs
    - D Flip Flops
    - Lots: ~5,000







# Next Time

- Studio